



**Physics Academy**  
www.physicsacademy.org

# Electric Circuits



Unit: 2 | Lecture: 9

**Solution of some selected problem**

Ohm's Law, Kirchhoff's Laws, Voltage Division,  
Current Division and Wye-Delta Transformations

**Dr. Hazem Falah Sakeek**  
**Al-Azhar University of Gaza**

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

{ 1 }

## Problems 2.2

Find the hot **resistance** of a light bulb rated 60W, 120 V.

$$P = 60W \quad v = 120V \quad R = ???$$

$$p = vi = i^2R = \frac{v^2}{R}$$

$$p = \frac{v^2}{R}$$

$$R = \frac{v^2}{p} = \frac{(120)^2}{60} = 240 \Omega$$

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

{ 2 }

## Problems 2.3

A bar of silicon is 4 cm long with a circular cross section. If the resistance of the bar is  $240\Omega$ , **what is the cross-sectional radius of the bar?**

$$l = 4 \text{ cm} \quad R = 240\Omega \quad \rho = 6.4 \times 10^2 \Omega \cdot \text{m} \quad r = ???$$

$$R = \rho \frac{l}{A} \quad \longrightarrow \quad A = \rho \frac{l}{R} \quad \longrightarrow \quad \pi r^2 = \rho \frac{l}{R}$$

$$r^2 = \rho \frac{l}{\pi R} \quad \longrightarrow \quad r^2 = 6.4 \times 10^2 \frac{4 \times 10^{-2}}{\pi \times 240}$$


$$r^2 = 0.0339 \quad \longrightarrow \quad r = 0.184 \text{ m}$$

( 3 )

## Problems 2.4

(a) Calculate **current  $i$**  in the circuit when the switch is in position 1.

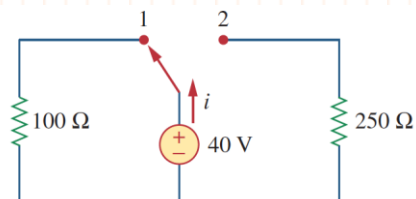(b) Find the **current  $i$**  when the switch is in position 2.



(a) switch is in position 1

$$i = \frac{v}{R} = \frac{40}{100} = 0.4 \text{ A}$$


(b) switch is in position 2

$$i = \frac{v}{R} = \frac{40}{350} = 0.16 \text{ A}$$

( 4 )
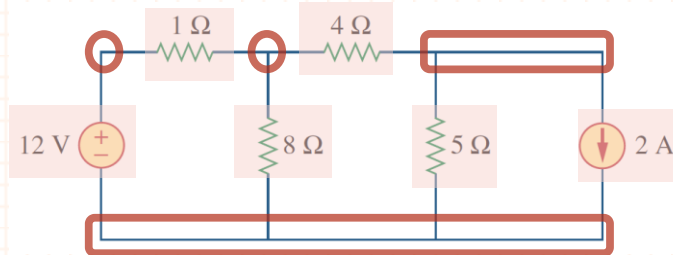
### Problems 2.7

Determine the **number of branches** and **nodes** in the circuit.



6 branches

4 nodes

### Problems 2.11

Calculate  $V_1$  and  $V_2$  in the circuit

Applying KVL to the left loop


$$-V_1 + 1 + 5 = 0$$

$$V_1 = 6 \text{ V}$$

Applying KVL to the right loop

$$-5 + 2 + V_2 = 0$$

$$V_2 = 3 \text{ V}$$

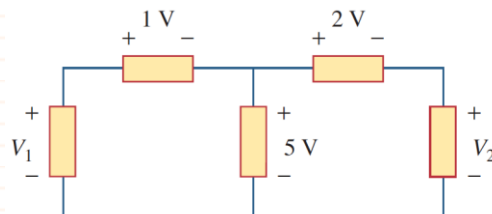

## Problems 2.15

Calculate  $v$  and  $i_x$  in the circuit

Applying KVL to the left loop


$$-10 + v + 4 = 0$$

$$v = 6 \text{ V}$$

Applying KVL to the right loop

$$-4 + 16 + 3i_x = 0$$

$$i_x = -4 \text{ A}$$

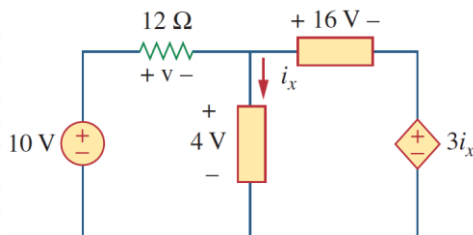

[ 7 ]

## Problems 2.16

Determine  $V_o$  in the circuit

Applying KVL to the circuit

$$-10 + (16 \times I) + (14 \times I) + 25 = 0$$


$$30I - 10 + 25 = 0$$

$$I = \frac{10 - 25}{30} = -0.5 \text{ A}$$

Applying KVL to the left loop

$$-10 + 16I + V_o = 0 \quad \longrightarrow \quad -10 + 16 \times (-0.5) + V_o = 0$$

$$V_o = 18 \text{ V}$$

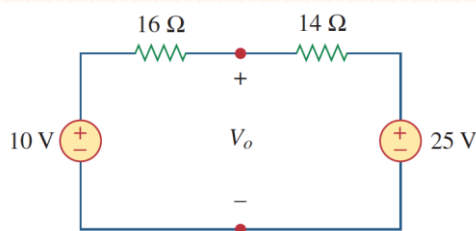

[ 8 ]


## Problems 2.20

Determine  $i_o$  in the circuit

Applying KVL to the circuit

$$-54 + 22i_o + 5i_o = 0$$

$$i_o = \frac{54}{27} = 2 \text{ A}$$

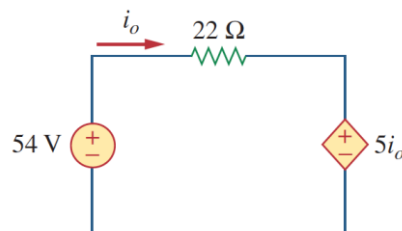

[ 9 ]

## Problems 2.26

For the circuit  $i_o = 3 \text{ A}$ , Calculate  $i_x$  and the total power absorbed by the entire circuit.


$$v_{16\Omega} = i_o 16 = 3 \times 16 = 48 \text{ V}$$

$$v_{16\Omega} = v_{2\Omega} = v_{4\Omega} = v_{8\Omega} = 48 \text{ V}$$

$$i_{2\Omega} = \frac{48}{2} = 24 \text{ A}$$

$$i_{4\Omega} = \frac{48}{4} = 12 \text{ A}$$
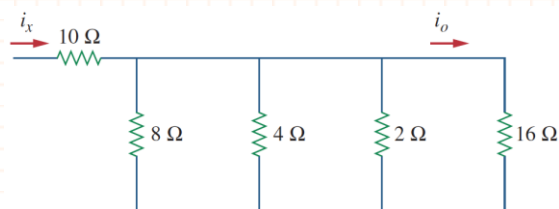
$$i_{8\Omega} = \frac{48}{8} = 6 \text{ A}$$



$$i_x = i_{2\Omega} + i_{4\Omega} + i_{8\Omega} + i_{16\Omega}$$

$$i_x = 24 + 12 + 6 + 3 = 45 \text{ A}$$

$$p = 45^2 \times 10 + 6^2 \times 8 + 12^2 \times 4 + 24^2 \times 2 + 3^2 \times 16$$

$$p = 22,356 \text{ W}$$

[ 10 ]

## Problems 2.27



Calculate  $I_o$  in the circuit

$$3\Omega || 6\Omega = \frac{3 \times 6}{3 + 6} = 2\Omega$$

Applying KVL to the circuit

$$-10 + (8 \times I_o) + 2 \times I_o = 0$$

$$I_o = \frac{10}{8 + 2} = 1 \text{ A}$$

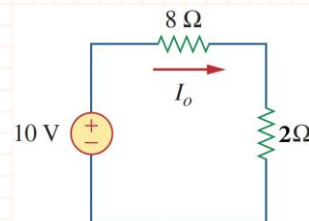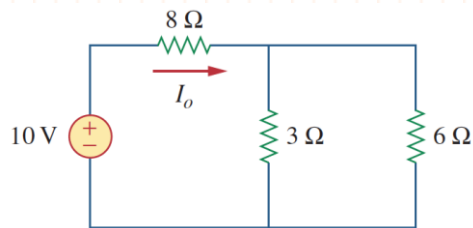

## Problems 2.29

All resistors in are  $5\Omega$  each. Find  $R_{eq}$

The last 2 resistor on the left are in series

$$5 + 5 = 10\Omega$$

$$10\Omega || 5\Omega = \frac{10 \times 5}{10 + 5} = 3.3\Omega$$

$$3.3\Omega \text{ in series with } 5\Omega = 8.3\Omega$$

$$8.3\Omega || 5\Omega = \frac{8.3 \times 5}{8.3 + 5} = 3.1\Omega$$

$$3.1\Omega \text{ in series with } 5\Omega = 8.1\Omega = R_{eq}$$

