



**Physics Academy**  
www.physicsacademy.org

# Electric Circuits



**Unit: 3 | Lecture: 15**  
**Solution of some selected problem**  
**Nodal analysis & Mesh analysis**

**Dr. Hazem Falah Sakeek**  
**Al-Azhar University of Gaza**

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

( 1 )

## Problems 3.2

**Obtain the node voltages in the circuit.**

Draw the current direction at each node

Apply KCL at node 1,

$$\frac{0 - v_1}{10} + \frac{0 - v_1}{5} = 6 + \frac{v_1 - v_2}{2}$$

$$-8v_1 + 5v_2 = 60 \quad (1)$$



Apply KCL at node 2,

$$3 + 6 + \frac{v_1 - v_2}{2} = \frac{v_2 - 0}{4}$$

$$-2v_1 + 3v_2 = 36 \quad (2)$$

Solve equations (1) & (2)

$$v_1 = 0 \quad \& \quad v_2 = 12$$

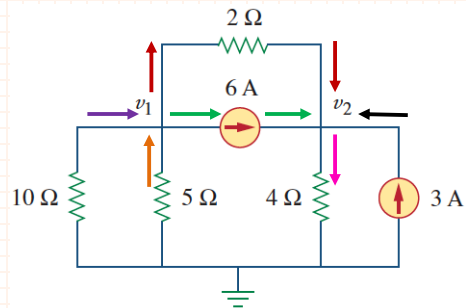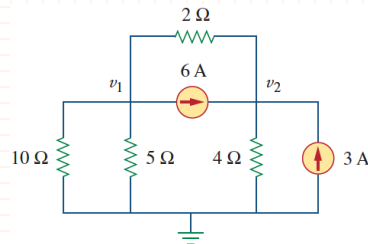

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

( 2 )

## Problems 3.3

Find the currents  $I_1$  through  $I_4$  and the voltage  $v_o$  in the circuit.We have **one nonreference** nodeApply **KCL**

$$I_1 + I_2 + I_3 + 20 + I_4 = 8$$

$$\frac{v_o}{10} + \frac{v_o}{20} + \frac{v_o}{30} + 20 + \frac{v_o}{60} = 8$$


$$v_o = -60 \text{ V}$$

$$I_1 = \frac{v_o}{10} = -6 \text{ A}$$

$$I_2 = \frac{v_o}{20} = -3 \text{ A}$$


$$I_3 = \frac{v_o}{30} = -2 \text{ A}$$

$$I_4 = \frac{v_o}{60} = -1 \text{ A}$$

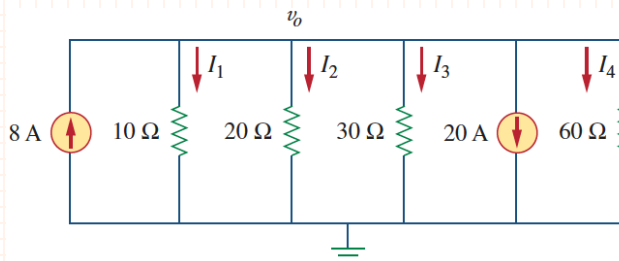

3

## Problems 3.4

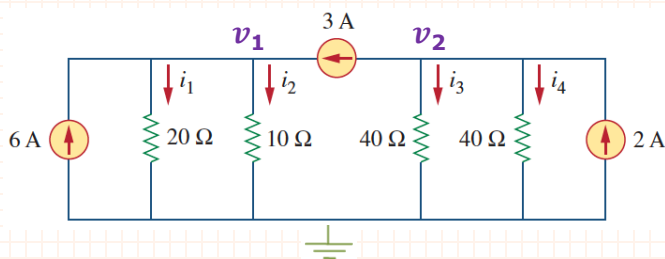Find the currents  $I_1$  through  $I_4$  and the voltage  $v_o$  in the circuit.We have **two nonreference** node around the current source 3 A.Apply **KCL** at node 1

$$6 + 3 = i_1 + i_2$$

$$6 + 3 = \frac{v_1}{20} + \frac{v_1}{10}$$

$$v_1 = 60 \text{ V}$$

Apply **KCL** at node 2

$$2 = 3 + i_3 + i_4$$

$$2 = 3 + \frac{v_2}{40} + \frac{v_2}{40}$$

$$v_2 = -20 \text{ V}$$

$$i_1 = \frac{v_1}{20} = \frac{60}{20} = 3 \text{ A}$$

$$i_2 = 6 \text{ A}$$

$$i_3 = -0.5 \text{ A}$$

$$i_4 = -0.5 \text{ A}$$

4

## Problems 3.5 (1)

Obtain  $v_o$  in the circuitApply KCL at node  $v_o$ 

$$I_1 + I_2 + I_0 = 0$$

but

$$v_o = -4000I_0 \quad \rightarrow \quad I_0 = -\frac{v_o}{4000}$$

Notice that

$$v_o - v_1 = 30$$



$$v_o + 2000I_1 = 30$$

$$\therefore I_1 = \frac{30 - v_o}{2000}$$

$$v_o - v_2 = 20$$

$$v_o + 5000I_2 = 20$$
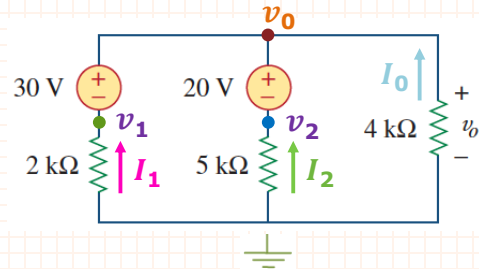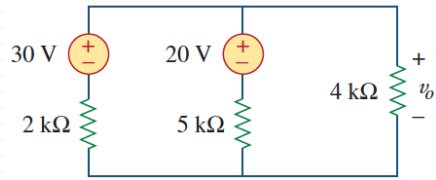
$$\therefore I_2 = \frac{20 - v_o}{5000}$$



5

## Problems 3.5 (2)

$$I_1 + I_2 + I_0 = 0$$


$$\frac{30 - v_o}{2} + \frac{20 - v_o}{5} - \frac{v_o}{4} = 0$$

$$\frac{10(30 - v_o)}{20} + \frac{4(20 - v_o)}{20} - \frac{5v_o}{20} = 0$$

$$300 - 10v_o + 80 - 4v_o - 5v_o = 0$$

$$380 - 19v_o = 0$$

$$v_o = 20 \text{ V}$$

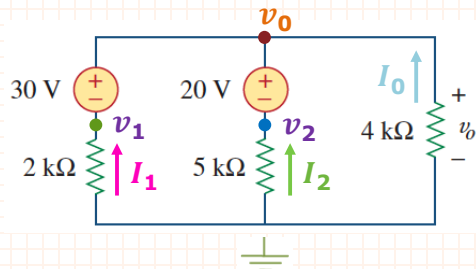

$$I_0 = -\frac{v_o}{4000}$$

$$I_1 = \frac{30 - v_o}{2000}$$

$$I_2 = \frac{20 - v_o}{5000}$$

6

## Problems 2.7

Apply nodal analysis to solve for  $V_x$  in the circuit.


Applying KCL to the circuit

$$2 = I_1 + I_2 + 0.2V_x$$

$$2 = \frac{V_x - 0}{10} + \frac{V_x - 0}{20} + 0.2V_x$$

$$40 = 2V_x + V_x + 4V_x$$

$$V_x = \frac{40}{7} = 5.714 \text{ V}$$

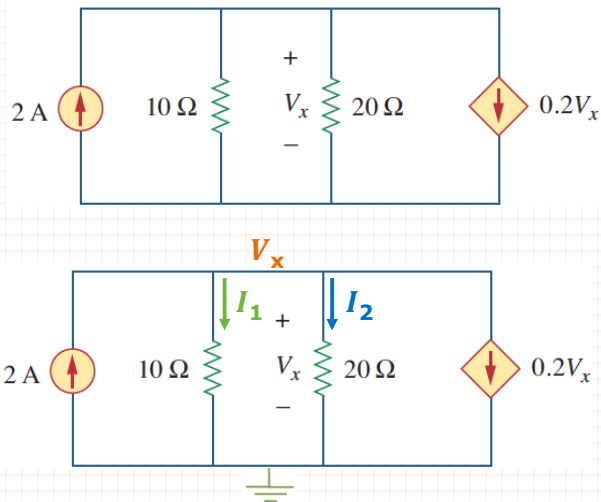

(7)

## Problems 2.8

Using nodal analysis, find  $v_o$  in the circuit.

Applying KCL to the circuit

$$I_1 + I_2 + I_3 = 0$$

$$\frac{v_1 - 0}{6 + 4} + \frac{(v_1 - 60) - 0}{20} + \frac{(v_1 - 5v_o) - 0}{20} = 0$$



$$\frac{v_1}{10} + \frac{v_1 - 60}{20} + \frac{v_1 - 5v_o}{20} = 0$$

$$4v_1 - 5v_o = 60$$

Using voltage divider to replace  $v_o$ 

$$v_o = \frac{4}{4 + 6} v_1 \quad \rightarrow \quad v_1 = \frac{10}{4} v_o$$
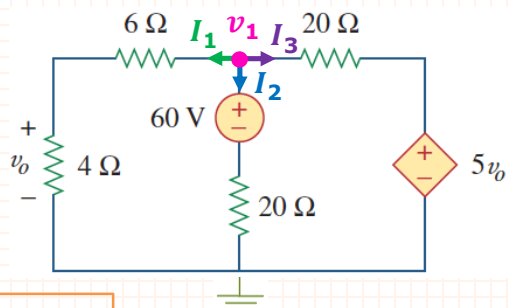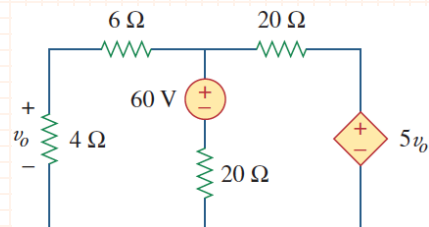
$$4 \times \frac{10}{4} v_o - 5v_o = 60 \quad \rightarrow \quad v_o = \frac{60}{5} = 12 \text{ V}$$



(8)

## Problems 2.10

Find  $I_o$  in the circuit.

At node 1  $\frac{v_1}{8} + 4 + \frac{v_1 - v_3}{1} = 0$   $\Rightarrow 9v_1 - 8v_3 = -32$  (1)

At node 2  $\frac{v_2 - 0}{2} + 2I_o = 4$  But  $I_o = \frac{v_1}{8}$

$$\frac{v_2}{2} + \frac{2v_1}{8} = 4 \Rightarrow v_1 + 2v_2 = 16$$
 (2)


At node 3  $\frac{v_1 - v_3}{1} + 2I_o = \frac{v_3}{4}$

$$v_1 - v_3 + \frac{2v_1}{8} = \frac{v_3}{4} \Rightarrow 5v_1 - 5v_3 = 0$$

$$\therefore v_1 = v_3$$
 (3)

Substitute eqn. (3) in eqn. (1)
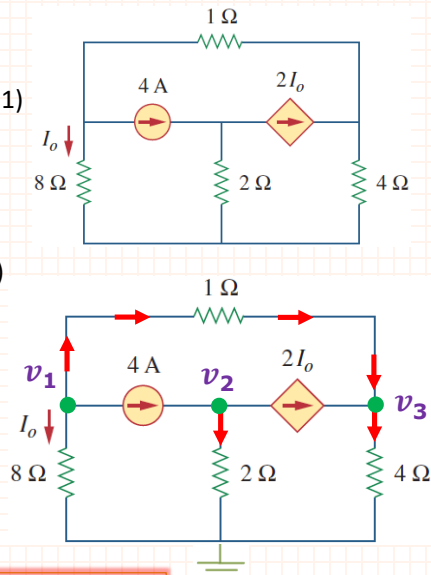
$$9v_1 - 8v_1 = -32 \Rightarrow v_1 = -32 \text{ V} \Rightarrow \therefore I_o = \frac{v_1}{8} = -4 \text{ A}$$



[ 9 ]

## Problems 2.12

Using nodal analysis, determine  $V_o$  in the circuit.

At node 1  $\frac{v_1 - 40}{20} + \frac{v_1}{20} + \frac{v_1 - v_2}{10} = 0$

$$v_1 - 40 + v_1 + 2v_1 - 2v_2 = 0$$

$$4v_1 - 2v_2 = 40$$
 (1)


At node 2  $\frac{v_1 - v_2}{10} + 4I_x = \frac{v_2}{10}$

But  $I_x = \frac{v_1}{20}$

$$v_1 - v_2 - 2v_1 = v_2$$

$$3v_1 = 2v_2 \Rightarrow v_1 = 0.666v_2$$
 (2)

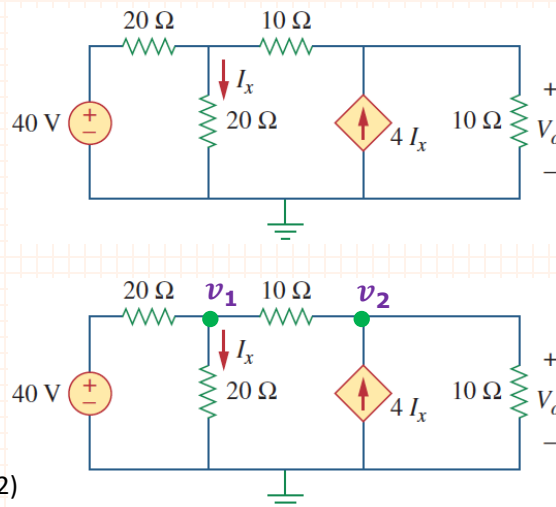Substitute eqn. (2) in eqn. (1)  $4 \times 0.666v_2 - 2v_2 = 40 \Rightarrow V_o = v_2 = 60 \text{ V}$



[ 10 ]