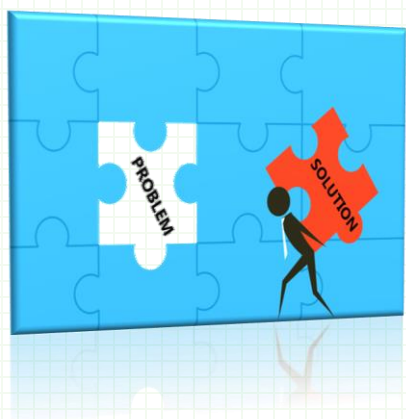




**Physics Academy**  
www.physicsacademy.org

# Electric Circuits



**Unit: 6 | Lecture: 30**

**Solution of some selected problem**

Capacitors and Inductors

**Dr. Hazem Falah Sakeek**

**Al-Azhar University of Gaza**

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

( 1 )

1

## Problems 6.1

If the voltage across a **7.5-F** capacitor is  $2te^{-3t}$  V find the current and the power.

**The current**

$$\begin{aligned} i &= C \frac{dv}{dt} \\ &= 7.5(2e^{-3t} - 6te^{-3t}) \\ &= 15(1 - 3t)e^{-3t} \text{ A} \end{aligned}$$

**The power**

$$\begin{aligned} p &= vi \\ &= 2te^{-3t} \times 15(1 - 3t)e^{-3t} \\ &= 30t(1 - 3t)e^{-6t} \text{ W} \end{aligned}$$

Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

( 2 )

2

## Problems 6.4

A current of  $4 \sin 4t$  A flows through a 5-F capacitor. Find the voltage  $v(t)$  across the capacitor given that  $v(0) = 1$  V.

The voltage  $v(t)$

$$\begin{aligned}
 v(t) &= \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0) \\
 &= \frac{1}{5} \int_0^t 4 \sin 4\tau d\tau + 1 \\
 &= \frac{4}{5} \left( \frac{-\cos 4\tau}{4} \right) \Big|_0^t + 1 \\
 &= -0.2 \cos 4t \Big|_0^t + 1 \\
 &= -0.2 \cos 4t - (-0.2 \cos 0) + 1 \\
 &= -0.2 \cos 4t + 0.2 + 1 \\
 &= 1.2 - 0.2 \cos 4t \text{ V}
 \end{aligned}$$

3

3

## Problems 6.12

A voltage of  $30e^{-2000t}$  V appears across a parallel combination of a 100-mF capacitor and a  $12\Omega$  resistor. Calculate the power absorbed by the parallel combination.

The power

$$p = vi$$

We have the voltage, so we need to find the current through the resistor  $i_R$  and the current in the capacitor  $i_C$ .

$$i_R = \frac{v}{R} = \frac{30e^{-2000t}}{12} = 2.5 e^{-2000t} \text{ A}$$

$$\begin{aligned}
 i_C &= C \frac{dv}{dt} = 100 \times 10^{-3} \frac{d30e^{-2000t}}{dt} \\
 &= 0.1 \times 30 \times (-2000) e^{-2000t} = -6000 e^{-2000t} \text{ A}
 \end{aligned}$$

The current

$$i = i_R + i_C = -5997.5 e^{-2000t} \text{ A}$$

The power

$$p = vi = -5997.5 e^{-2000t} \times 30e^{-2000t} = -180 e^{-4000t} \text{ W}$$

4

4

**Problems 6.13**

Find the voltage across the capacitors in the circuit under dc conditions.

Under dc conditions, the circuit is as shown

$$i_1 = \frac{60}{40 + 10 + 20} = 0.857 \text{ A}$$



$$i_2 = 0$$

$$v_1 = 40 \times i_1 = 34.3 \text{ V}$$

Apply KVL to find  $v_2$ 

$$v_2 - 60 + 20i_1 = 0$$

$$v_2 = 42.86 \text{ V}$$

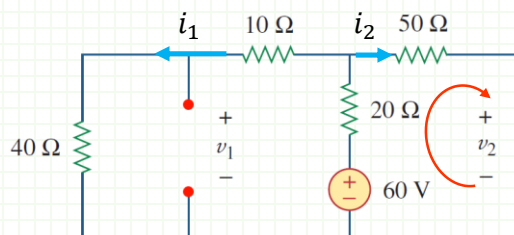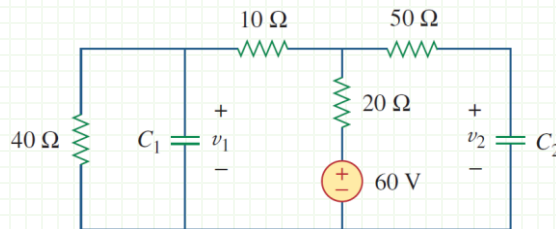

5

**Problems 6.14**

Series-connected 20-pF and 60-pF capacitors are placed in parallel with series-connected 30-pF and 70-pF capacitors. Determine the equivalent capacitance.

$$20 \text{ pF is in series with } 60\text{pF} = \frac{20 \times 60}{20 + 60} = 15 \text{ pF}$$

$$30\text{-pF is in series with } 70\text{pF} = \frac{30 \times 70}{30 + 70} = 21 \text{ pF}$$

$$15\text{pF is in parallel with } 21\text{pF} = 15 + 21 = 36 \text{ pF}$$

6

## Problems 6.16

The equivalent capacitance at terminals  $a-b$  in the circuit is  $30 \mu\text{F}$ . Calculate the value of  $C$ .


$$C_{eq} = 14 + \frac{C \times 80}{C + 80} = 30$$

$$\frac{C \times 80}{C + 80} = 16$$

$$80C = 16C + 1280$$

$$64C = 1280$$

$$C = 20 \mu\text{F}$$

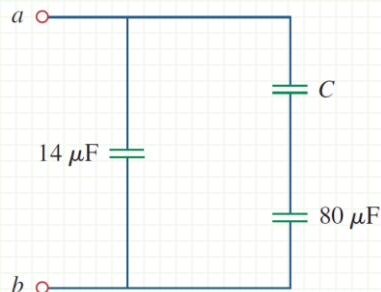


[ 7 ]

7
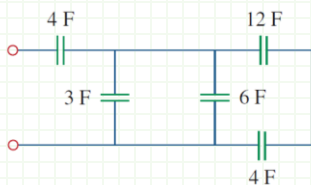
## Problems 6.17

Determine the equivalent capacitance for each of the circuits.



4F in series with 12F


$$= \frac{4 \times 12}{4 + 12} = 3 \text{ F}$$

3F in parallel with 6F and 3F

$$= 3 + 6 + 3 = 12 \text{ F}$$

4F in series with 12F
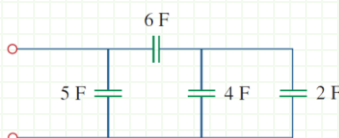
$$C_{eq} = \frac{4 \times 12}{4 + 12} = 3 \text{ F}$$



2F in parallel with 4F


$$= 2 + 4 = 6 \text{ F}$$

6F in series with 6F

$$= \frac{6 \times 6}{6 + 6} = 3 \text{ F}$$

3F in parallel with 5F

$$C_{eq} = 3 + 5 = 8 \text{ F}$$

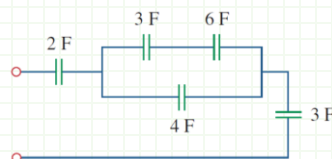

3F in series with 6F

$$= \frac{3 \times 6}{3 + 6} = 2 \text{ F}$$

2F in parallel with 4F

$$= 2 + 4 = 6 \text{ F}$$

6F, 2F, and 3F are in series

$$\frac{1}{C_{eq}} = \frac{1}{6} + \frac{1}{2} + \frac{1}{3} = 1$$

$$C_{eq} = 1 \text{ F}$$

[ 8 ]

8

## Problems 6.34

The current through a **10-mH** inductor is  $10e^{-t/2}$  A. Find the voltage and the power at  $t=3$ s.

## The voltage

$$v = L \frac{di}{dt}$$

$$v = 10 \times 10^{-3} \frac{d(10e^{-t/2})}{dt}$$

$$= 10 \times 10^{-3} \times 10 \times \frac{-1}{2} e^{-t/2}$$

$$= -50 \times 10^{-3} e^{-t/2}$$

$$v(3) = -50 \times 10^{-3} e^{-3/2}$$

$$= -0.011157 \text{ V}$$

## The power

$$p = vi$$

$$= -50 \times 10^{-3} e^{-t/2} \times 10e^{-t/2}$$

$$= -500 \times 10^{-3} e^{-t}$$

$$p(3) = -500 \times 10^{-3} e^{-3}$$

$$p(3) = -0.025 \text{ W}$$

[9]

9

## Problems 6.35

An inductor has a linear change in current from **50 mA** to **100 mA** in **2 ms** and induces a voltage of **160 mV**. Calculate the value of the inductor.

$$v = L \frac{di}{dt}$$

$$L = \frac{v}{\frac{di}{dt}}$$

$$L = \frac{160 \times 10^{-3}}{\frac{(100 - 50)10^{-3}}{2 \times 10^{-3}}}$$

$$L = 6.4 \times 10^{-3} \text{ H}$$

[10]

10

### Problems 6.39

The voltage across a 200-mH inductor is given by  $v(t) = 3t^2 + 2t + 4$  V for  $t > 0$ . Determine the current  $i(t)$  through the inductor. Assume that  $i(0) = 1$  A.

$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$i = \frac{1}{200 \times 10^{-3}} \int_0^t 3t^2 + 2t + 4 dt + i(0)$$

$$i = 5 t^3 + t^2 + 4t \Big|_0^t + 1$$

$$i(t) = 5t^3 + 5t^2 + 20t + 1 \text{ A}$$

[11]

11

### Problems 6.46

Find  $v_C$ ,  $i_L$  and the energy stored in the capacitor and inductor in the circuit under dc conditions.

Under dc conditions, the circuit is as shown



Using current division to find  $i_L$

$$i_L = \frac{4}{4+2} \times 3 = 2 \text{ A}$$

$$v_C = 0 \text{ V}$$

$$W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 0.5 \times 2^2 = 1 \text{ J}$$
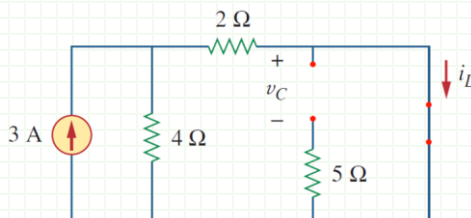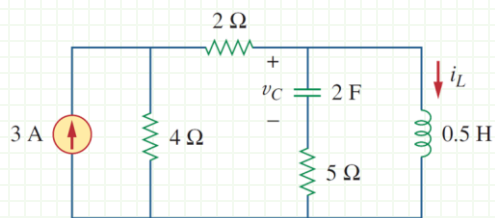
$$W_C = \frac{1}{2} C v_C^2 = 0 \text{ J}$$




[12]

12

## Problems 6.48


Under steady-state dc conditions, find  $i$  and  $v$  in the circuit.

Under dc conditions, the circuit is as shown

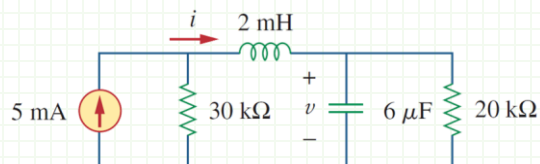Using current division to find  $i$ 

$$i = \frac{30}{30 + 20} \times 5 = 3 \text{ mA}$$
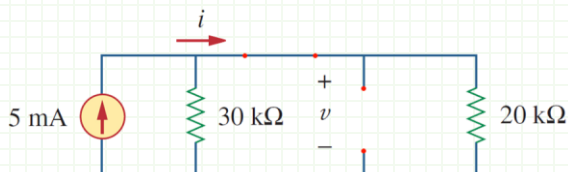
$$v = 20 \times i = 20 \times 3 = 60 \text{ V}$$



[13]

13

## Problems 6.51

Determine  $L_{eq}$  at terminals  $a$ - $b$  of the circuit


$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30}$$

$$\frac{1}{L} = \frac{1}{10}$$

$$L = 10$$

$$L_{eq} = 10 || (25 + 10)$$
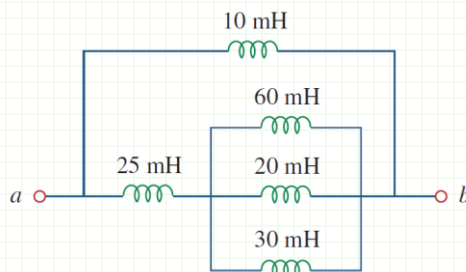
$$L_{eq} = \frac{10 \times 35}{10 + 35} = 7.778 \text{ mH}$$



[14]

14

## Problems 6.53

Find  $L_{eq}$  at the terminals of the circuit

5 mH is in parallel with 8 mH and 12 mH

$$= 5 || (8 + 12)$$

$$= \frac{5 \times (8 + 12)}{5 + (8 + 12)} = 4 \text{ mH}$$

6 mH is in parallel with 4 mH and 8 mH

$$= 6 || (4 + 8)$$


$$= \frac{6 \times (4 + 8)}{6 + (4 + 8)} = 4 \text{ mH}$$

8 mH is in parallel with 4 mH and 4 mH

$$= 8 || (4 + 4) = 4 \text{ mH}$$

6 mH, 10 mH and 4 mH are in series

$$L_{eq} = 6 + 10 + 4 = 20 \text{ mH}$$

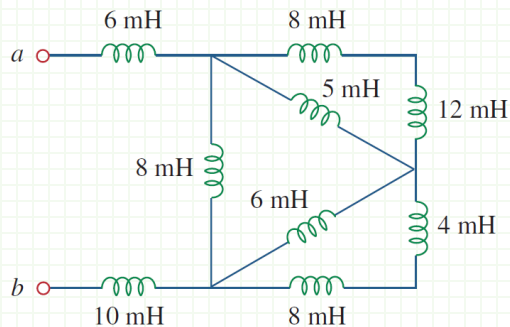

[15]

15

## Problems 6.61

Consider the circuit. Find: (a)  $L_{eq}$  and  $i_1(t)$ ,  $i_2(t)$  if  $i_s = 3e^{-t}$  mA (b)  $v_o(t)$ , (c) energy stored in the 20-mH inductor at  $t=1$  s.(a)  $L_{eq}$ 

$$L_{eq} = 20 || (4 + 6) = \frac{20 \times 10}{20 + 10} = 6.667 \text{ mH}$$

Using current division to find  $i_1(t)$  and  $i_2(t)$ 

$$i_1(t) = \frac{10}{10 + 20} \times i_s = \frac{1}{3} \times 3e^{-t} = e^{-t} \text{ mA}$$

$$i_2(t) = \frac{20}{10 + 20} \times i_s = \frac{2}{3} \times 3e^{-t} = 2e^{-t} \text{ mA}$$

(b)  $v_o(t)$ 

$$v_o = L_{eq} \frac{di_s}{dt}$$

$$= 6.667 \times 10^{-3} (-3 \times 10^{-3} \times e^{-t})$$


$$= -20 \times 10^{-6} e^{-t} \text{ V}$$

(c) energy stored in the 20-mH inductor at  $t=1$  s.

$$W = \frac{1}{2} Li_1^2$$

$$= \frac{1}{2} \times 20 \times 10^{-3} \times e^{-2} \times 10^{-6}$$

$$= 1.353 \times 10^{-9} \text{ J}$$

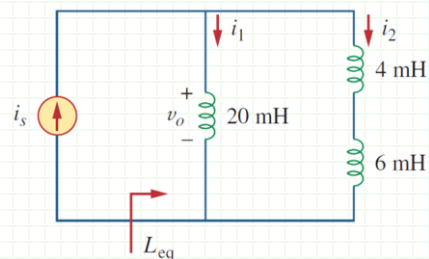

[16]

16