



Physics Academy

www.physicsacademy.org

Electric Circuits


Unit: 9 | Lecture: 34

Sinusoids and Phasors

Impedance and Admittance

Dr. Hazem Falah Sakeek

Al-Azhar University of Gaza

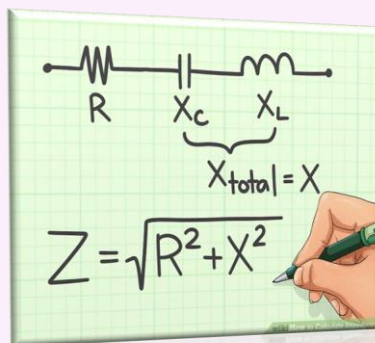


Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

(1)

1

Sinusoids and Phasors

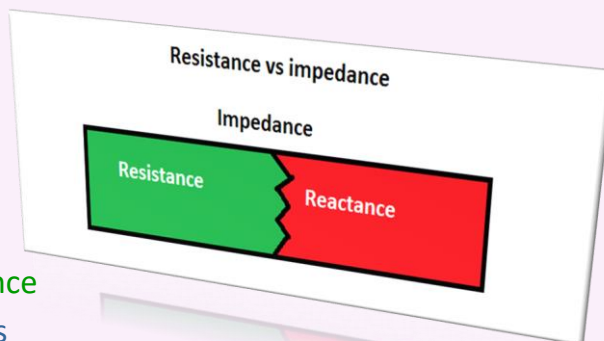- 9.1 Introduction
- 9.2 Sinusoids' features
- 9.3 Phasors
- 9.4 Phasor relationships for circuit elements
- 9.5 Impedance and admittance
- 9.7 Impedance combinations



Dr. Hazem Falah Sakeek | www.hazemsakeek.net | www.physicsacademy.org

(2)

2

9.5 Impedance (1)

The voltage-current relations for the three passive elements as

$$\begin{array}{lll} \mathbf{V} = R\mathbf{I} & \mathbf{V} = j\omega L\mathbf{I} & \mathbf{V} = \frac{\mathbf{I}}{j\omega C} \\ \text{resistor} & \text{inductor} & \text{capacitor} \end{array}$$

These equations may be written in terms of the ratio of the phasor voltage to the phasor current as

$$\frac{\mathbf{V}}{\mathbf{I}} = R \qquad \frac{\mathbf{V}}{\mathbf{I}} = j\omega L \qquad \frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C}$$

Ohm's law in phasor form for any type of element as

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} \qquad \text{or} \qquad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

where \mathbf{Z} is a frequency-dependent quantity known as *impedance*, measured in ohms.

9.5 Impedance (2)

The impedance \mathbf{Z} of a circuit is the ratio of the phasor voltage \mathbf{V} to the phasor current \mathbf{I} , measured in ohms (Ω).

Extreme case (1)

When $\omega = 0$ i.e. for dc sources

$$\mathbf{Z}_L = 0 \quad \text{and} \quad \mathbf{Z}_C \rightarrow \infty$$



confirming that the inductor acts like a short circuit, while the capacitor acts like an open circuit.

Extreme case (2)

When $\omega \rightarrow \infty$ i.e. for high frequencies

$$\mathbf{Z}_L \rightarrow \infty \quad \text{and} \quad \mathbf{Z}_C = 0$$

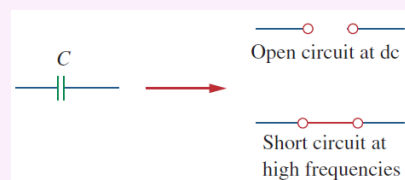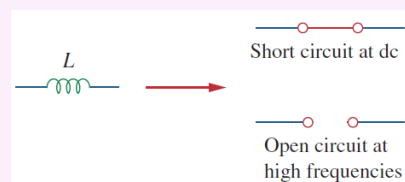indicating that the inductor is an open circuit to high frequencies, while the capacitor is a short circuit.



9.5 Impedance (3)

The impedance may be expressed in rectangular form as

$$\mathbf{Z} = R + jX$$

Where $R = \text{Re } \mathbf{Z}$ is the resistance and $X = \text{Im } \mathbf{Z}$ is the reactance

The reactance X may be positive or negative.

Thus, impedance $\begin{cases} \mathbf{Z} = R + jX & \text{is said to be } \textit{inductive} \text{ or lagging since current} \\ & \text{lags voltage} \\ \mathbf{Z} = R - jX & \text{is capacitive or leading because current leads} \\ & \text{voltage.} \end{cases}$

5

9.5 Impedance (4)

The impedance may also be expressed in polar form as

$$\mathbf{Z} = |\mathbf{Z}| \angle \theta$$

Therefore, the impedance is

$$\mathbf{Z} = R + jX = |\mathbf{Z}| \angle \theta$$

where

$$|\mathbf{Z}| = \sqrt{R^2 + X^2} \quad \theta = \tan^{-1} \frac{X}{R}$$

and

$$R = |\mathbf{Z}| \cos \theta \quad X = |\mathbf{Z}| \sin \theta$$

6

9.5 Admittance (1)

The admittance Y is the reciprocal of impedance, measured in siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V}$$

The admittance Y is the ratio of the phasor current through it to the phasor voltage across it

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

7

9.5 Admittance (2)

As a complex quantity the admittance Y may written as

$$Y = G + jB$$

Where $G = \text{Re } Y$ is the conductance and $B = \text{Im } Y$ is the susceptance.

Admittance, conductance, and susceptance are all expressed in the unit of siemens (or mhos).

8

9.5 Admittance (3)

Relation between admittance and impedance

$$\mathbf{Z} = R + jX$$

impedance

$$\mathbf{Y} = G + jB$$

admittance

$$\mathbf{Y} = \frac{1}{\mathbf{Z}}$$

$$G + jB = \frac{1}{R + jX}$$

$$G + jB = \frac{1}{R + jX} \times \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

Equating the real and imaginary parts gives

$$G = \frac{R}{R^2 + X^2}$$

$$B = -\frac{X}{R^2 + X^2}$$

showing that $G \neq 1/R$ as it is in resistive circuits. Of course, if $X = 0$, then $G = 1/R$.

[9]

9


Example 9.9 (1)

Find $v(t)$ and $i(t)$ in the circuit

From the voltage source $v_s = 10 \cos 4t$

$$v_s = 10 \cos 4t$$

$$V_s = 10 \angle 0$$

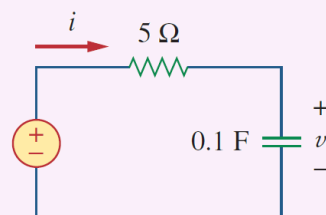

The impedance is

$$\mathbf{Z} = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \Omega$$

Hence the current

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10 \angle 0}{5.6 \angle -26.5^\circ}$$

$$\mathbf{I} = 1.78 \angle 26.57^\circ \text{ A}$$

$$(5 - j2.5) \rightarrow r \angle \phi$$

$$r = \sqrt{5^2 + 2.5^2} = 5.6$$

$$\phi = \tan^{-1} \frac{-2.5}{5} = -26.57^\circ$$

[10]

10

Example 9.9 (2)

The voltage across the capacitor is


$$\begin{aligned} \mathbf{V} = \mathbf{I}\mathbf{Z}_C &= \frac{\mathbf{I}}{j\omega C} = \frac{1.78\angle 26.57^\circ}{j \times 4 \times 0.1} \\ &= \frac{1.78\angle 26.57^\circ}{0.4\angle 90^\circ} \\ &= 4.4\angle -63.42^\circ \text{ V} \end{aligned}$$

Converting \mathbf{I} and \mathbf{V} to the time domain, we get

$$i(t) = 1.789 \cos(4t + 26.57^\circ) \text{ A}$$

$$v(t) = 4.47 \cos(4t - 63.43^\circ) \text{ V}$$

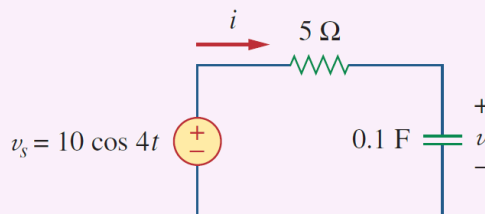Notice that $i(t)$ leads $v(t)$ by 90 as expected.




[11]


11

Problems to Solve by yourself

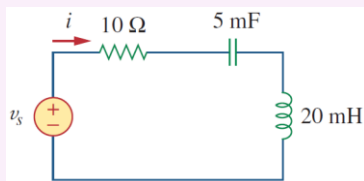
- (1) Find current i in the circuit when $v_s(t) = 50 \cos 200t \text{ V}$.



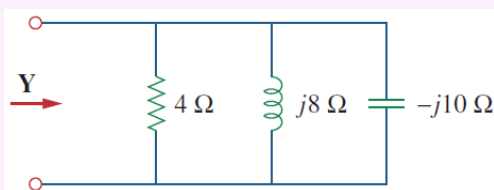
- (2) Determine the admittance \mathbf{Y} for the circuit



- (3) Find $v(t)$ in the RLC circuit

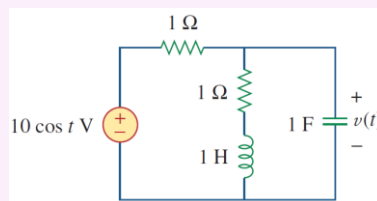

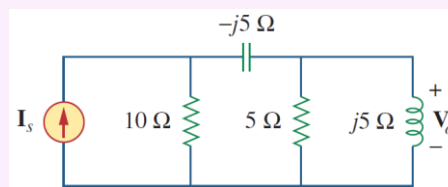- (4) If $V_o = 8\angle 30^\circ \text{ V}$ in the circuit, find \mathbf{I}_s .



[12]

12