




Physics Academy

www.physicsacademy.org

## General Physics II

Electrostatic: Principles & Applications

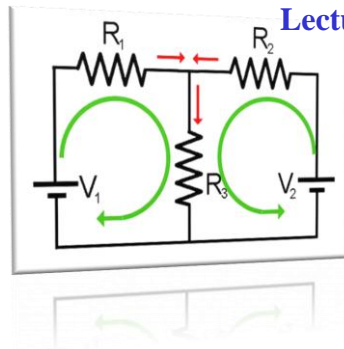

Lecture (20): Direct Current Circuits


**Kirchhoff's Rules**

Dr. Hazem Falah Sakeek

Al-Azhar University of Gaza
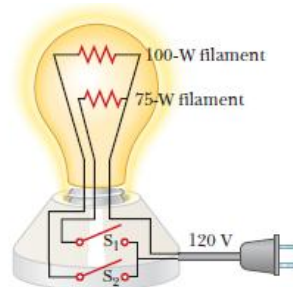
## Direct Current Circuits

- Electromotive Force
- Finding the current in a simple circuit
- **Kirchhoff's Rules**
- **Single-Loop Circuit**
- **Multi-Loop Circuit**
- **Problems**



سنعامل في هذا الفصل مع الدوائر الكهربائية التي تحتوي على بطارية ومقاومة. سنقوم بتحليل هذه الدوائر الكهربائية معتمدين على قاعدة كيرشوف **Kirchhoff's rule** لحساب التيار الكهربائي المار في كل عنصر من عناصر الدائرة الكهربائية. وبداية سنتعرف على مفهوم القوة الدافعة الكهربائية **Electromotive force**.

## Kirchhoff's Rules

A practical electrical circuit is usually complicated system of many electrical elements. Kirchhoff extended Ohm's law to such systems, and gave two rules, which together enabled the current in any part of the circuit to be calculated.

### Statements of Kirchhoff's Rules

(1) The algebraic sum of the currents entering any junction must equal the sum of the currents leaving that junction.

$$\sum_i I_i = 0 \quad \text{at the junction}$$

(2) The algebraic sum of the changes in potential difference across all of the elements around any closed circuit loop must be zero.

$$\sum_i \Delta V_i = 0 \quad \text{for the loop circuit}$$


*Note that the first Kirchhoff's rule is for the current and the second for the potential difference.*

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

3
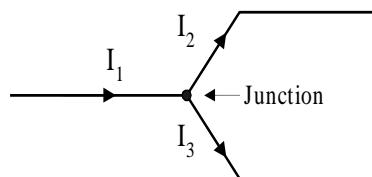
## Kirchhoff's Rules

Applying the first rule on the junction shown below



$$I_1 = I_2 + I_3$$


Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

4


## Kirchhoff's Rules

Applying the second rule on the following cases

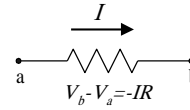
(1) If a resistor is traversed in the direction of the current, the change in potential difference across the resistor is  $-IR$ .



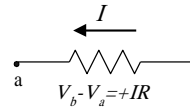
(2) If a resistor is traversed in the direction opposite the current, the change in potential difference across the resistor is  $+IR$ .



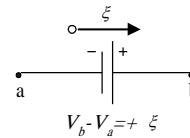(3) If a source of  $emf$  is traversed in the direction of the  $emf$  (from - to + on the terminal), the change in potential difference is  $+$ .



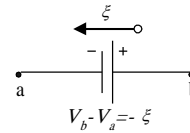(4) If a source of  $emf$  is traversed in the direction opposite the  $emf$  (from + to - on the terminal), the change in potential difference is  $-$ .



Dr. Hazem Falah Sakeek www.hazemsakeek.com & www.physicsacademy.org

5

## Hints for solution of problems using kirchhoff's rules

لاستخدام قاعدة كيرشوف يجب اتباع الخطوات التالية:

1. حدد اتجاه القوة الدافعة الكهربائية  $emf$  لكل بطارية في الدائرة الكهربائية بسهم متجه من القطب السالب إلى القطب الموجب للبطارية.
2. حدد اتجاه التيار الكهربائي لكل عنصر من عناصر الدائرة الكهربائية مثل المقاومة بافتراض اتجاه محدد للتيار حتى تتمكن من تطبيق قاعدة كيرشوف. فإذا كان الحل النهائي يظهر إشارة موجبة للتيار يكون الاتجاه المفترض صحيحاً، أما إذا ظهرت إشارة التيار سالبة فإن قيمة التيار صحيحة، ولكن اتجاه التيار في الاتجاه المعاكس للاتجاه المفترض.
3. نطبق القاعدة الأولى لكيرشوف عند العقدة الموجودة في الدائرة الكهربائية بحيث تكون إشارة التيارات الداخلة على العقدة موجبة والخارجة من العقدة سالبة.
4. نطبق القاعدة الثانية لكيرشوف على مسار مغلق محدد لكل فرع من أفرع الدائرة الكهربائية ونراعي التغير في فرق الجهد على كل عنصر من عناصر الدائرة الكهربائية إذا كان سالباً أو موجباً.
5. نحل المعادلات الرياضية التي نتجت من تطبيق الخطوتين (3) و(4) حلاً جبرياً.

Dr. Hazem Falah Sakeek www.hazemsakeek.com & www.physicsacademy.org


6

## Single-loop Circuit

In a single-loop circuit there is **no junctions** and the current is the same in all elements of the circuit, therefore we use **only the second Kirchhoff rule**.
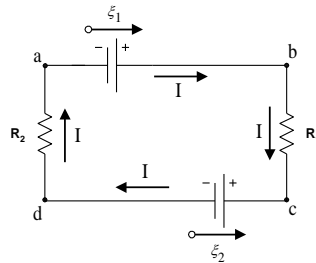
### Example (1)

Two battery are connected in opposite in a circuit contains two resistors as shown in figure 8.6 the *emf* and the resistance are  $\xi_1=6\text{v}$ ,  $\xi_2=12\text{v}$ ,  $R_1= 8\Omega$ , and  $R_2=10\Omega$ . (a) Find the current in the circuit. (b) What is the power dissipated in each resistor?



Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

7

## Solution


If we assume the current in the circuit is in the clockwise direction (*abcda*). Applying the second Kirchhoff's rule along arbitrary loop (*abcda*) we get

$$\sum_i \Delta V_i = 0$$

$$+\xi_1 - IR_1 - \xi_2 + IR_2 = 0$$

Solving for the current we get
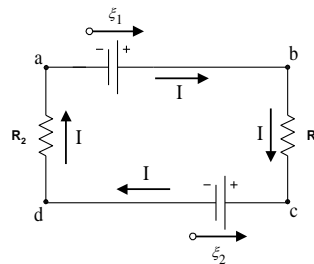
$$I = \frac{\xi_1 - \xi_2}{R_1 + R_2} = \frac{6 - 12}{8 + 10} = -\frac{1}{3} \text{ A}$$



The -ve sign of the current indicates that the correct direction of the current is opposite the assumed direction *i.e.* along the loop (*adba*)

The power dissipated in  $R_1$  and  $R_2$  is

$$P_1 = I^2 R_1 = 8/9 \text{ W}$$

$$P_2 = I^2 R_2 = 10/9 \text{ W}$$


In this example the battery  $\xi_2$  is being charged by the battery  $\xi_1$ .

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

8
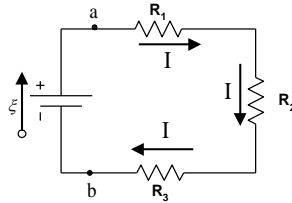
## Example (2)

Three resistors are connected in series with battery as shown in the figure, apply second Kirchhoff's rule to (a) Find the equivalent resistance and (b) find the potential difference between the points  $a$  and  $b$ .



### Solution

Applying second Kirchhoff's rule in clockwise direction we get

$$-IR_1 - IR_2 - IR_3 + \xi = 0$$

$$I = \frac{\xi}{R_1 + R_2 + R_3}$$

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

9

$$\therefore I = \frac{\xi}{R}$$

therefore,

$$R = R_1 + R_2 + R_3$$

To find the potential difference between points  $a$  and  $b$   $V_{ab} (=V_a - V_b)$  we use the second Kirchhoff's rule along a direction starting from point  $(b)$  and finish at point  $(a)$  through the resistors. We get

$$V_b + IR = V_a$$

Where  $R$  is the equivalent resistance for  $R_1$ ,  $R_2$  and  $R_3$

$$V_{ab} = V_a - V_b = +IR$$

The +ve sign for the answer means that  $V_a > V_b$

Substitute for the current  $I$  using the equation  $I = \frac{\xi}{R}$

we get

$$V_{ab} = \xi$$


This means that the potential difference between points  $a$  and  $b$  is equal to the *emf* in the circuit (when the internal resistance of the battery is neglected).

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

10
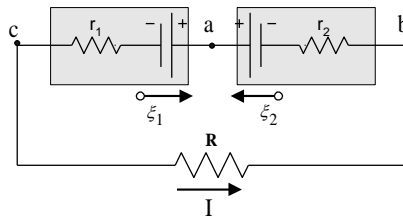
## Example (3)

In the circuit shown in the figure let  $\xi_1$  and  $\xi_2$  be 2v and 4v, respectively;  $r_1$ ,  $r_2$  and  $R$  be  $1\Omega$ ,  $2\Omega$ , and  $5\Omega$ , respectively. (a) What is the current in the circuit? (b) What is the potential difference  $V_a - V_b$  and  $V_a - V_c$ ?



### Solution

$$-\xi_2 + Ir_2 + IR + Ir_1 + \xi_1 = 0$$

Solving the equation for the current we get

$$I = \frac{\xi_2 - \xi_1}{R + r_1 + r_2} = \frac{4 - 2}{5 + 1 + 2} = +0.25A$$

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

11

The potential difference  $V_a - V_b$  we apply second Kirchhoff's rule starting at point  $b$  to finishing at point  $a$ .

$$V_a - V_b = -Ir_2 + \xi_2 = (-0.25 \times 2) + 4 = +3.5v$$

The potential difference  $V_a - V_c$  we apply second Kirchhoff's rule starting at point  $c$  to finishing at point  $a$ .


$$V_a - V_c = +\xi_1 + Ir_1 = +2 + (-0.25 \times 1) = +2.25v$$

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

12
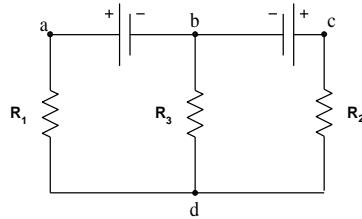
## Multi-loop Circuit

Some circuits involving more than one current loop, such as the one shown in the figure. Here we have a circuit with three loops: a left inside loop, a right inside loop, and an outside loop.



In the circuit shown above there are two junctions  $b$  and  $d$  and three branches connecting these junctions. These branches are  $bad$ ,  $bcd$ , and  $bd$ . The problem here is to find the currents in each branch.


A general method for solving multi-loop circuit problem is to apply Kirchhoff's rules.

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)


13

You should always follow these steps:

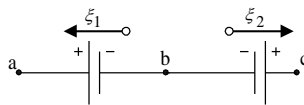(1) Assign the direction for the  $emf$  from the -ve to the +ve terminal of the battery.



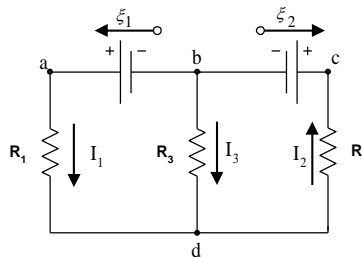(2) Assign the direction of the currents in each branch assuming arbitrary direction.



After solving the equations the +ve sign of the current means that the assumed direction is correct, and the -ve sign for the current means that the opposite direction is the correct one.

Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

14

(3) Chose one junction to apply the first Kirchhoff's rule.

$$\sum_i I_i = 0$$

At junction  $d$  current  $I_1$  and  $I_3$  is approaching the junction and  $I_2$  leaving the junction therefore we get this equation

$$I_1 + I_3 - I_2 = 0 \quad (1)$$

(4) For the three branches circuit assume there are two single-loop circuits and apply the second Kirchhoff's rule on each loop.


For loop a on the left side starting at point b we get

$$+\xi_1 - I_1 R_1 + I_3 R_3 = 0 \quad (2)$$

For loop b on the left side starting at point b we get

$$- I_3 R_3 - I_2 R_2 - \xi_2 = 0 \quad (3)$$

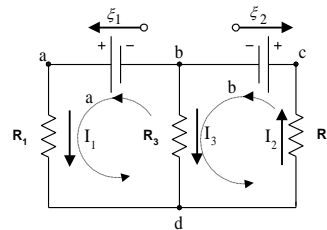Equations (1), (2), and (3) can be solved to find the unknowns currents  $I_1$ ,  $I_2$ , and  $I_3$ .



Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

15

## Example (4)

In the circuit shown in the figure, find the unknown current  $I$ , resistance  $R$ , and emf  $\xi$ .

### Solution

At junction a we get this equation

$$I + 1 - 6 = 0$$

Therefore the current

$$I = 5A$$

To determine  $R$  we apply the second Kirchhoff's rule on the loop (a), we get


$$18 - 5R + 1 \times 2 = 0$$

$$R = 4\Omega$$

To determine  $\xi$  we apply the second Kirchhoff's rule on the loop (b), we get

$$\xi + 6 \times 2 + 1 \times 2 = 0$$

$$\xi = -14V$$

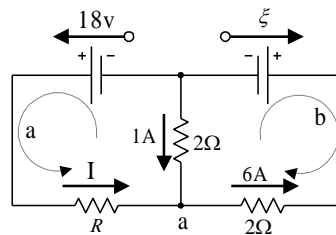


Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

16




## Problem to solve by your self

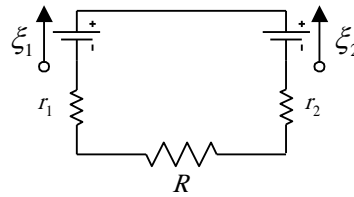1. (a) In the figure what value must  $R$  have if the current in the circuit is to be  $0.0010\text{A}$ ? Take  $\xi_1=2.0\text{V}$ ,  $\xi_2=3.0\text{V}$ , and  $r_1=r_2=3.0\Omega$ .  
 (b) What is the rate of thermal energy transfer in  $R$ ?



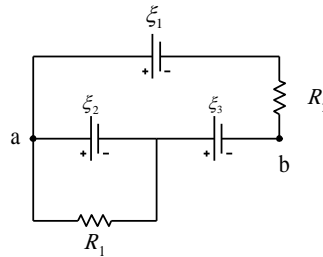2. In the figure find the current in each resistor and the potential difference between  $a$  and  $b$ . Put  $\xi_1=6.0\text{V}$ ,  $\xi_2=5.0\text{V}$ ,  $\xi_3=4.0\text{V}$ ,  $R_1=100\Omega$  and  $R_2=50\Omega$ .




Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)


17

## Problem to solve by your self

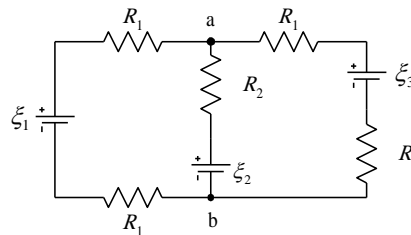3. (a) Find the three currents in the figure. (b) Find  $V_{ab}$ . Assume that  $R_1=1.0\Omega$ ,  $R_2=2.0\Omega$ ,  $\xi_1=2.0\text{V}$ , and  $\xi_2=\xi_3=4.0\text{V}$ .



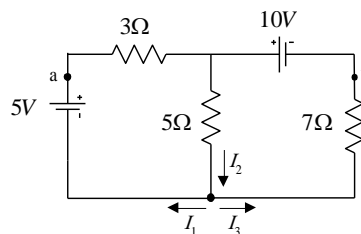4. (a) Find the potential difference between points  $a$  and  $b$  in the circuit in the figure. (b) Find the currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit



Dr. Hazem Falah Sakeek [www.hazemsakeek.com](http://www.hazemsakeek.com) & [www.physicsacademy.org](http://www.physicsacademy.org)

18